
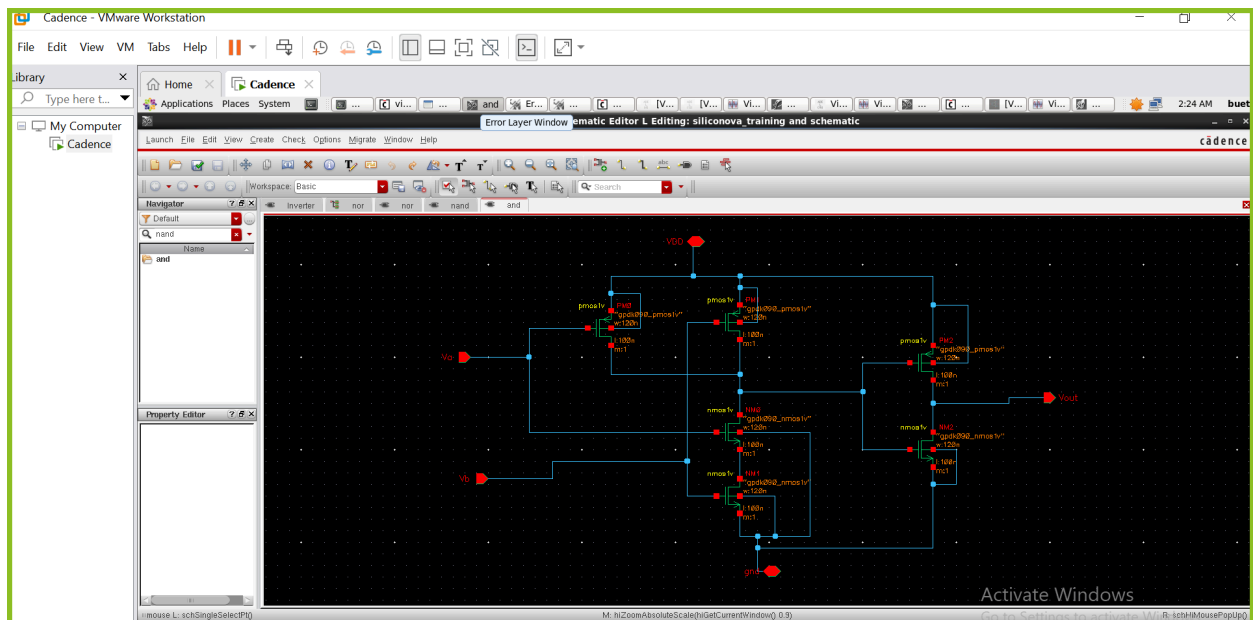



# AND Gate

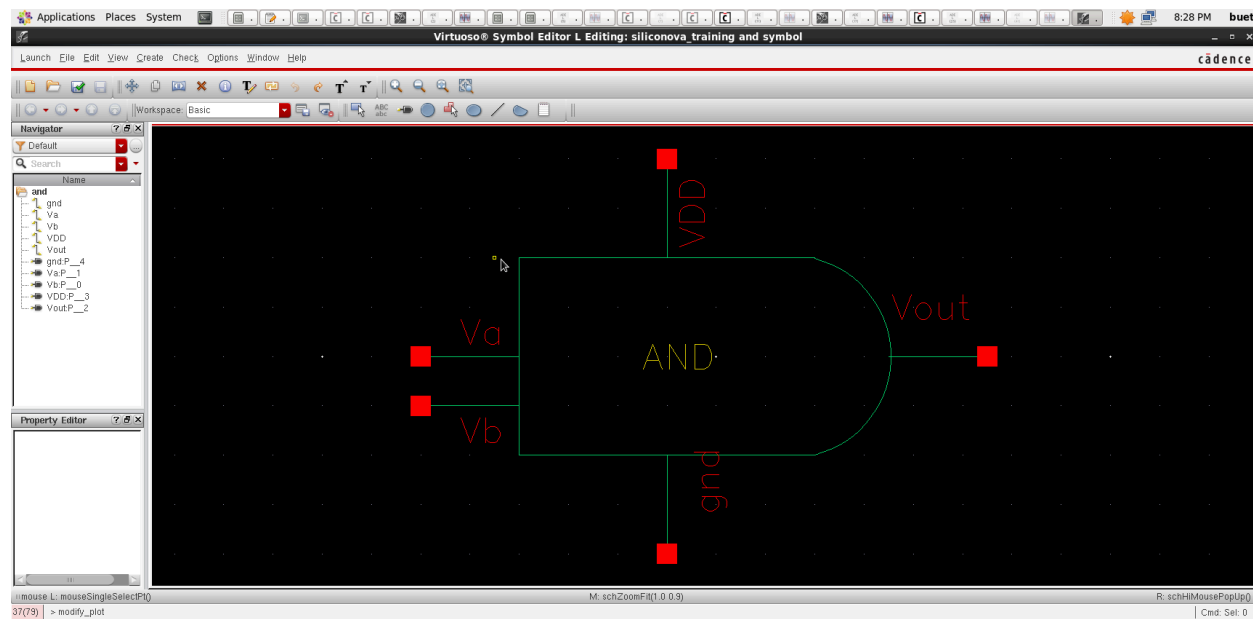


Symbol of AND Gate:




## Testbench Diagram:

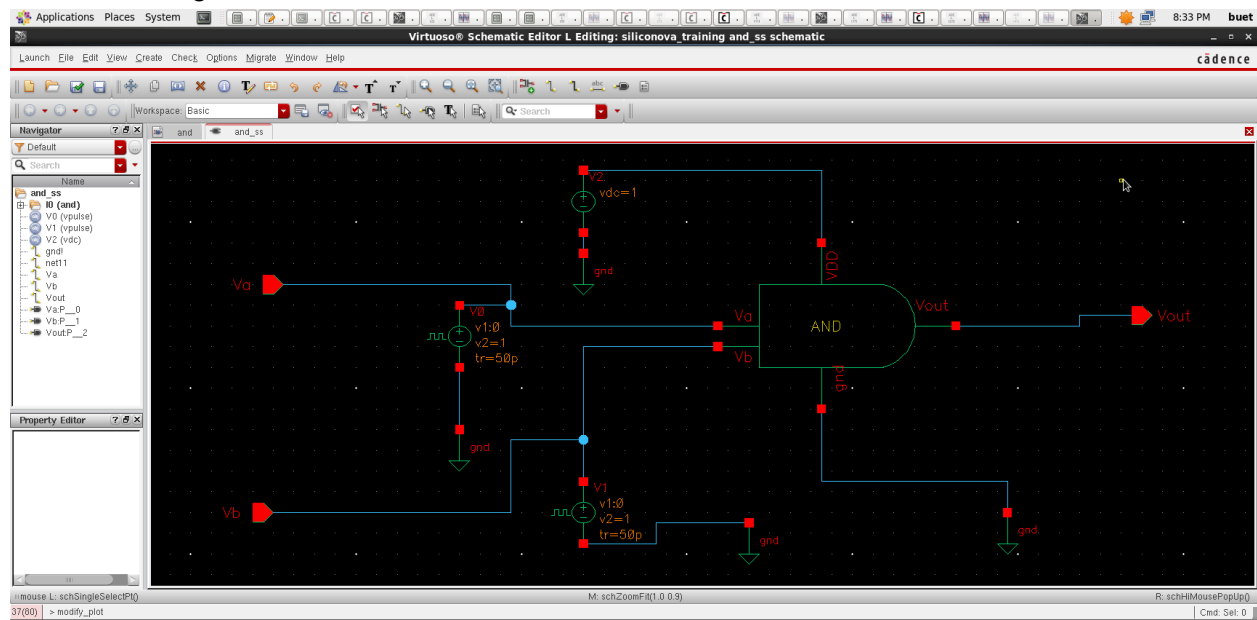

 
## Output of Testbench Diagram in Transient Response:




# NAND Gate

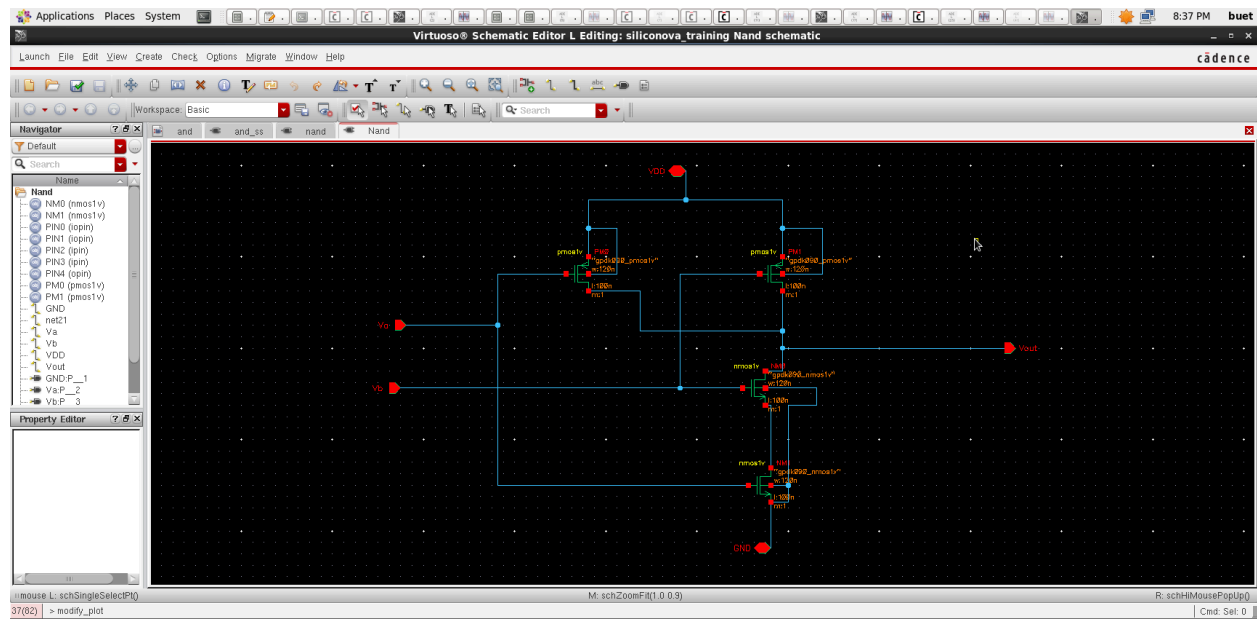


## Symbol of NAND Gate:

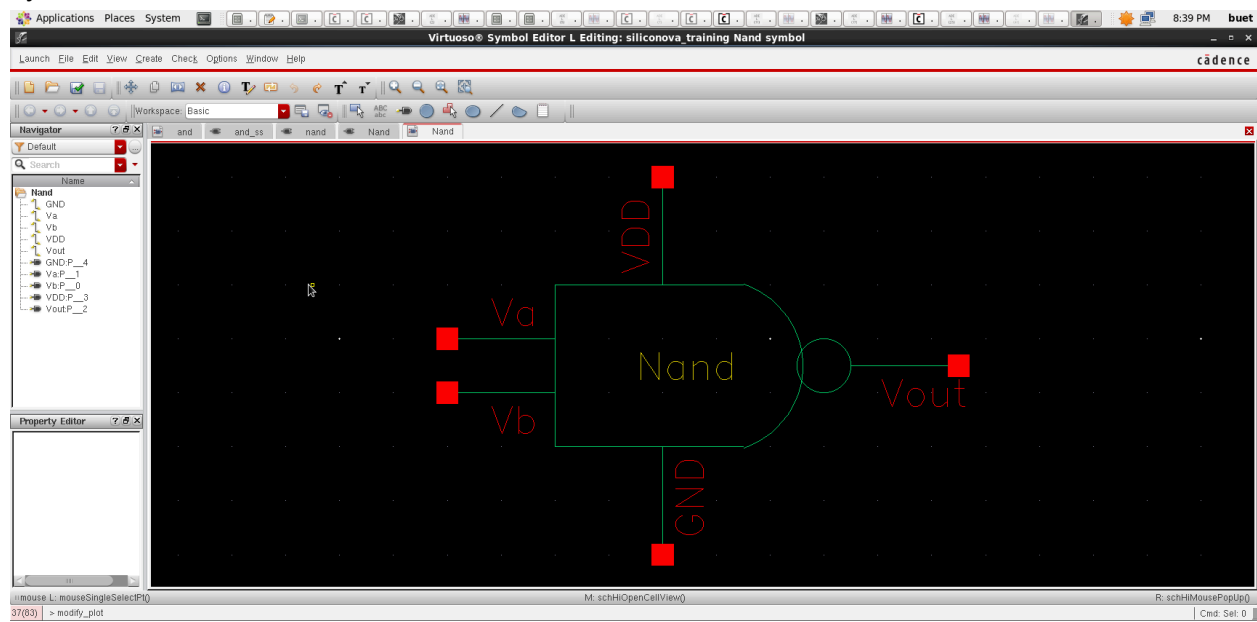


Schematic Diagram of testbench:

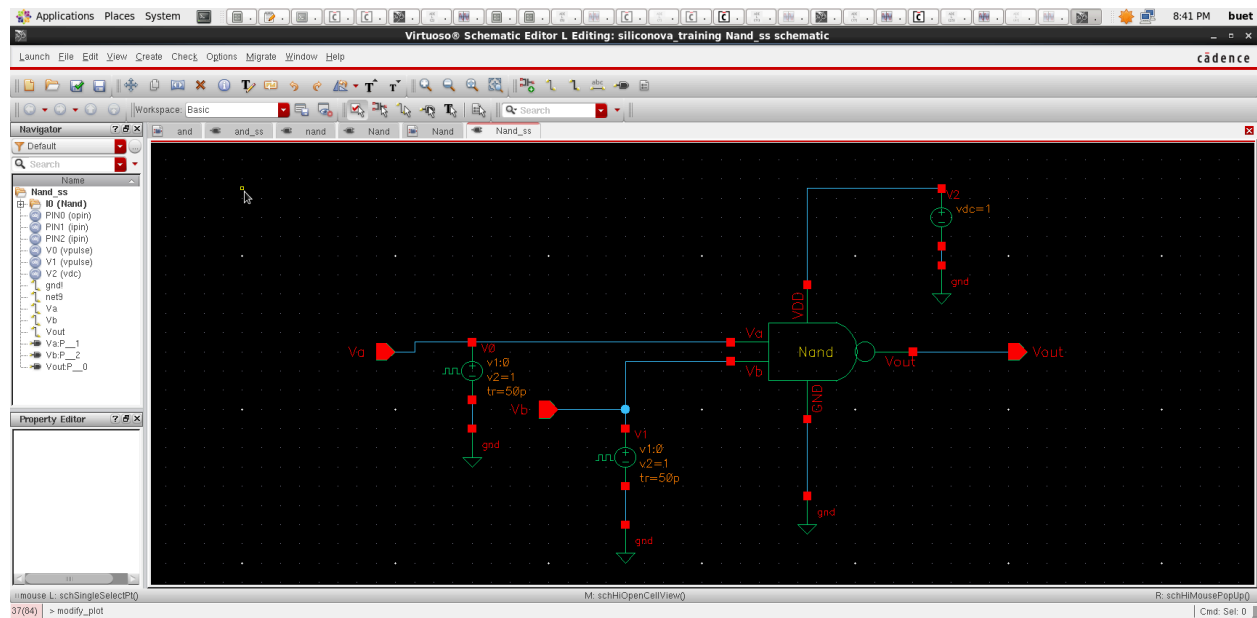


Output:

 


## Layout: layout of Nand gate

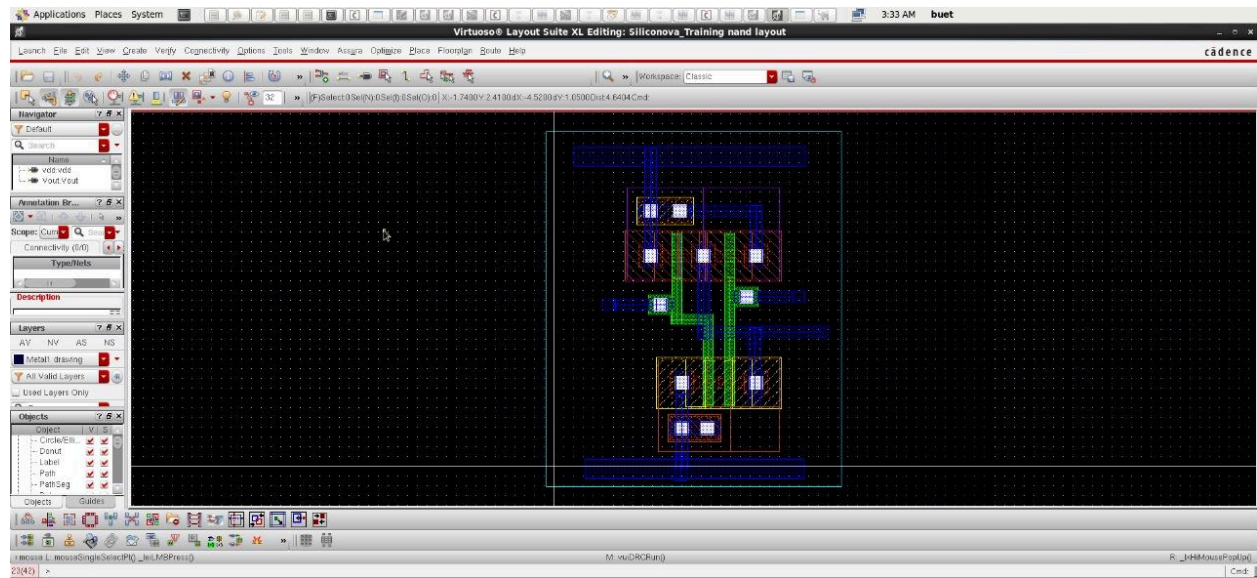


# NOR Gate

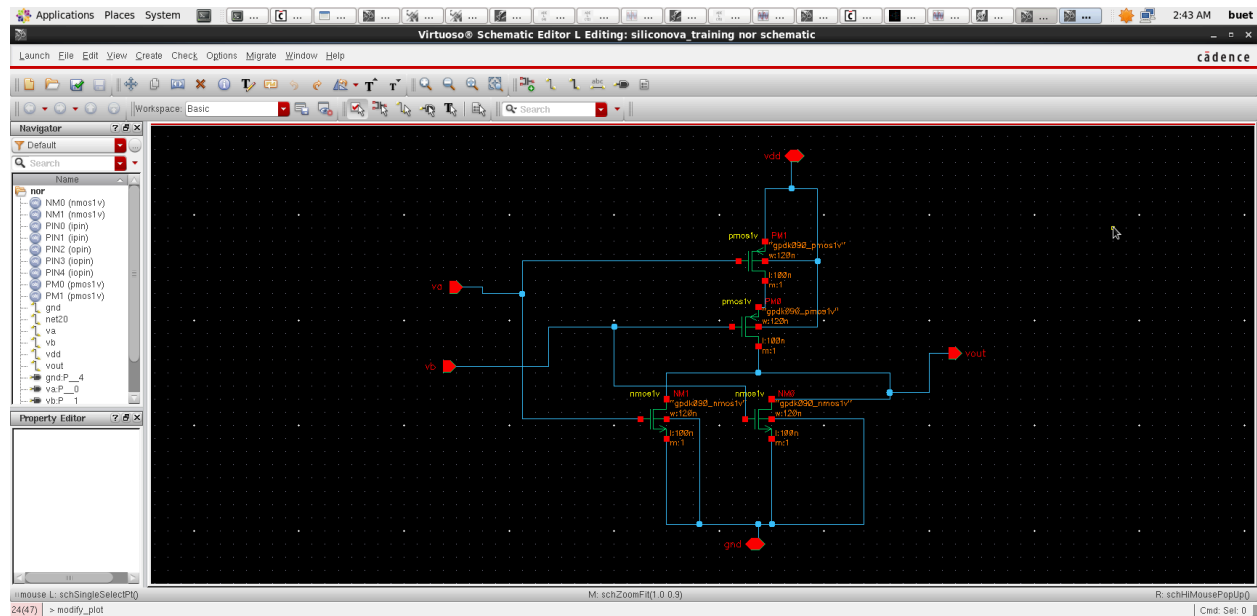


## Symbol of NOR Gate:

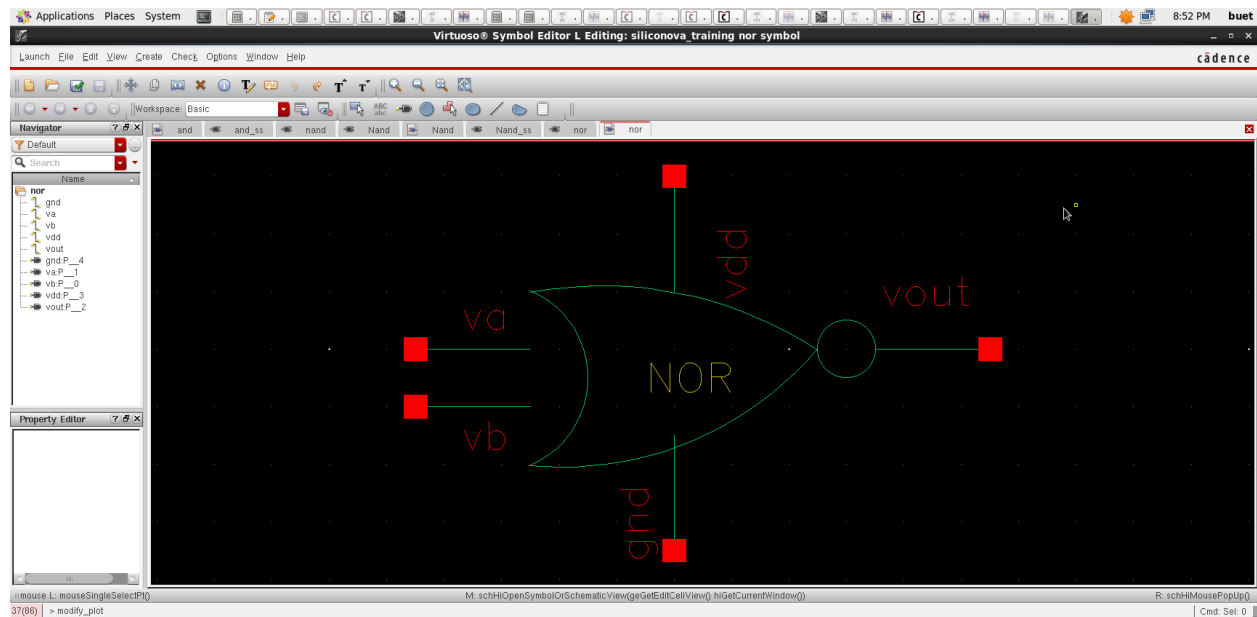


Schematic diagram of testbench:

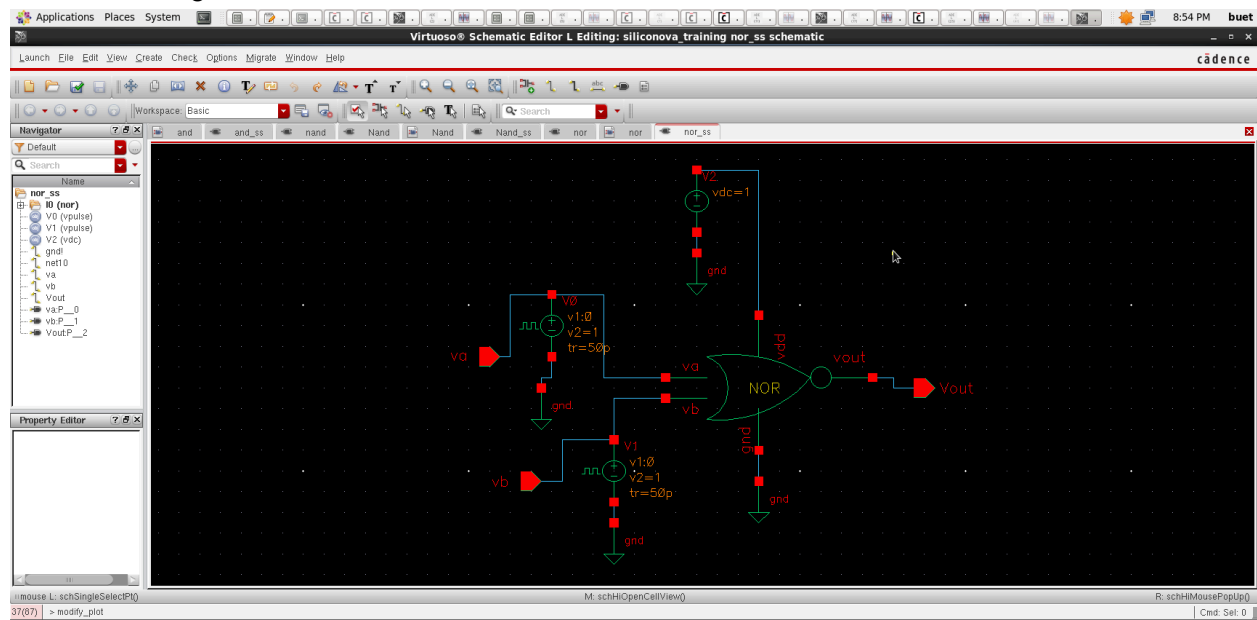

Output:

 


Layout:

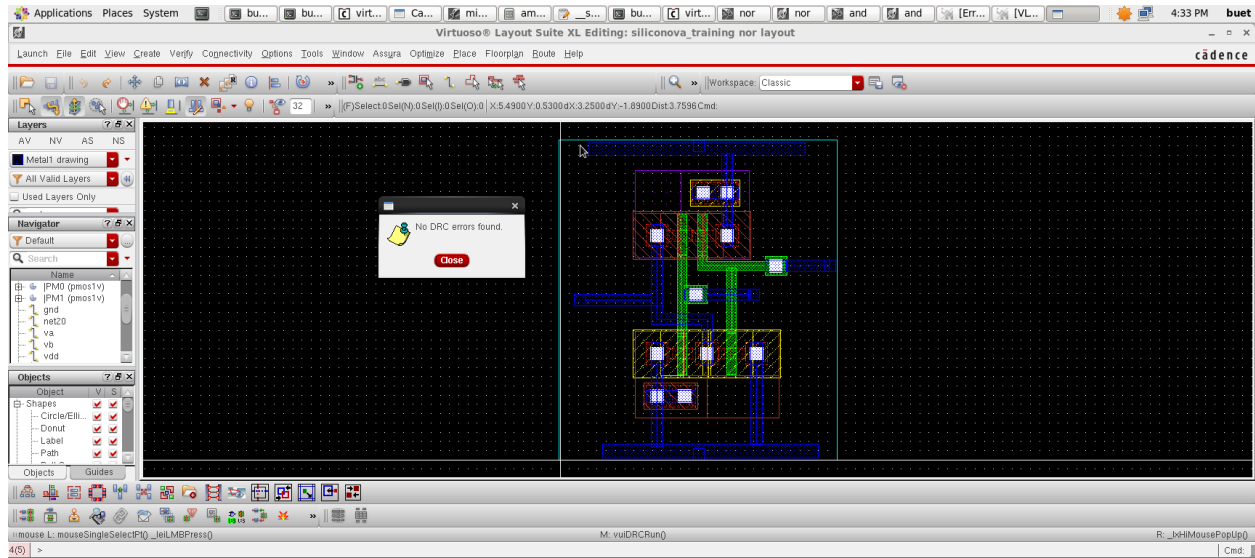





# OR Gate

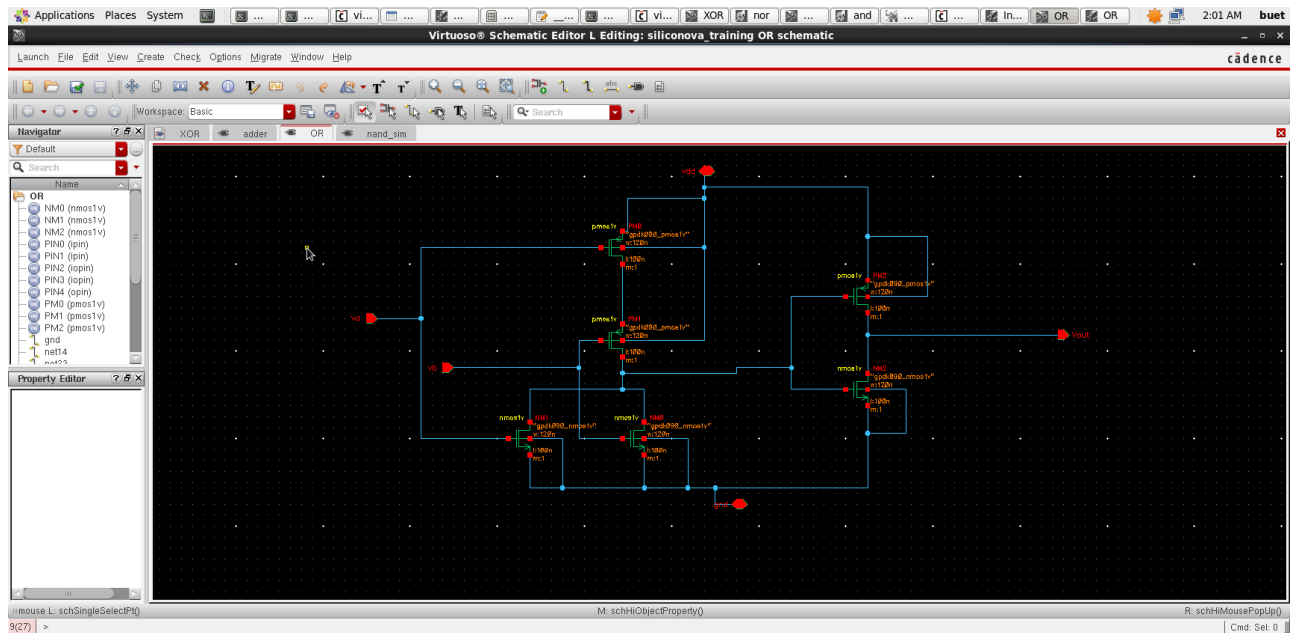


Symbol:

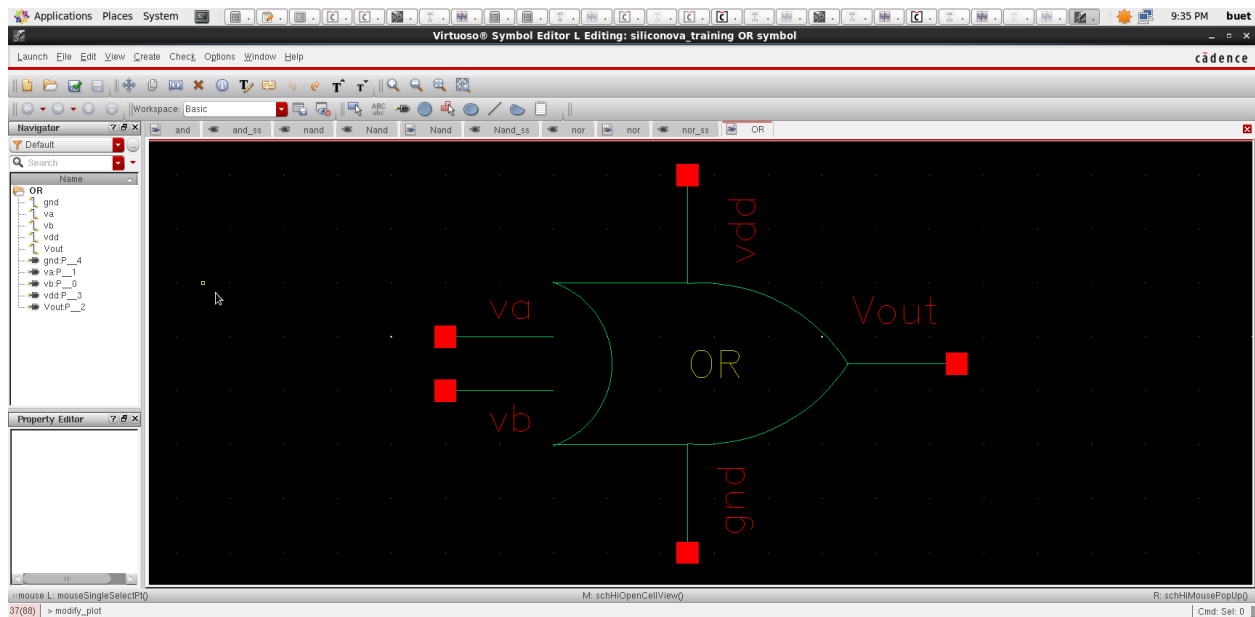


## Testbench diagram of OR Gate:

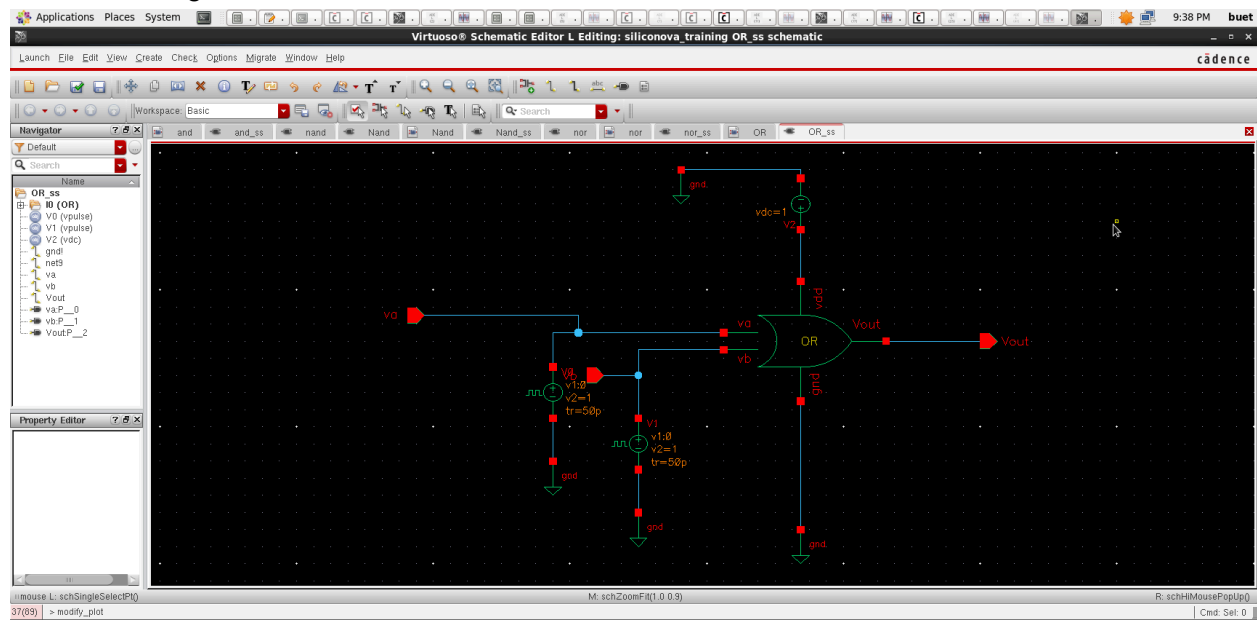

## Output:


 


# ADDER

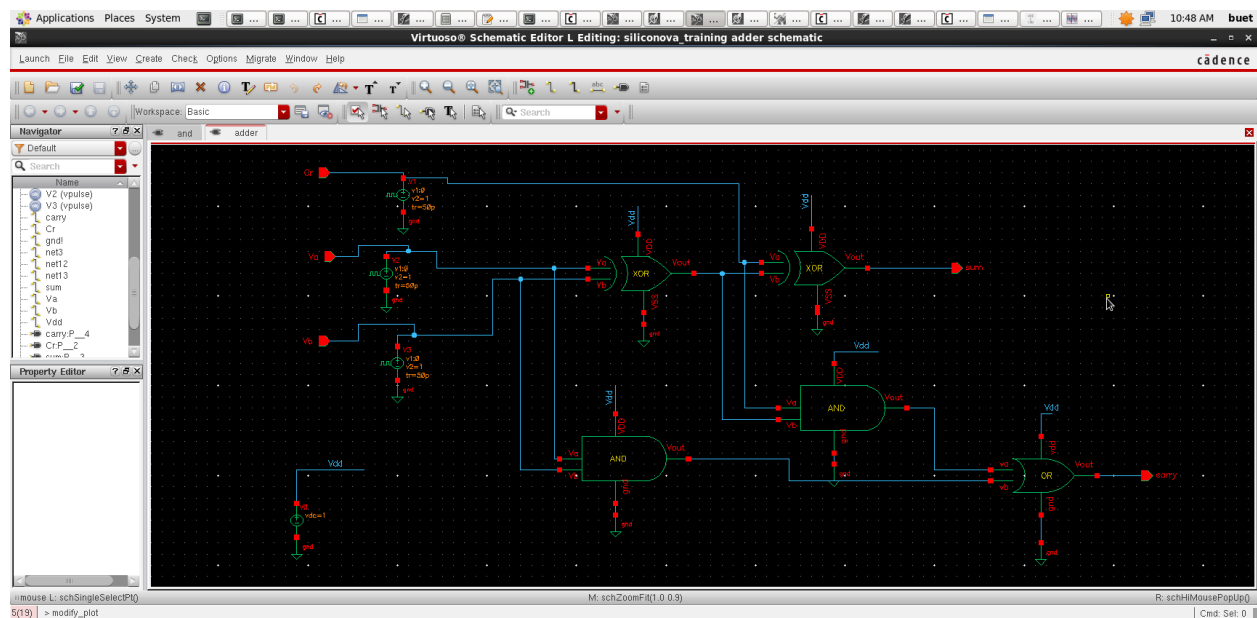


# 6T SRAM


Schematic of 6 T SRAM:

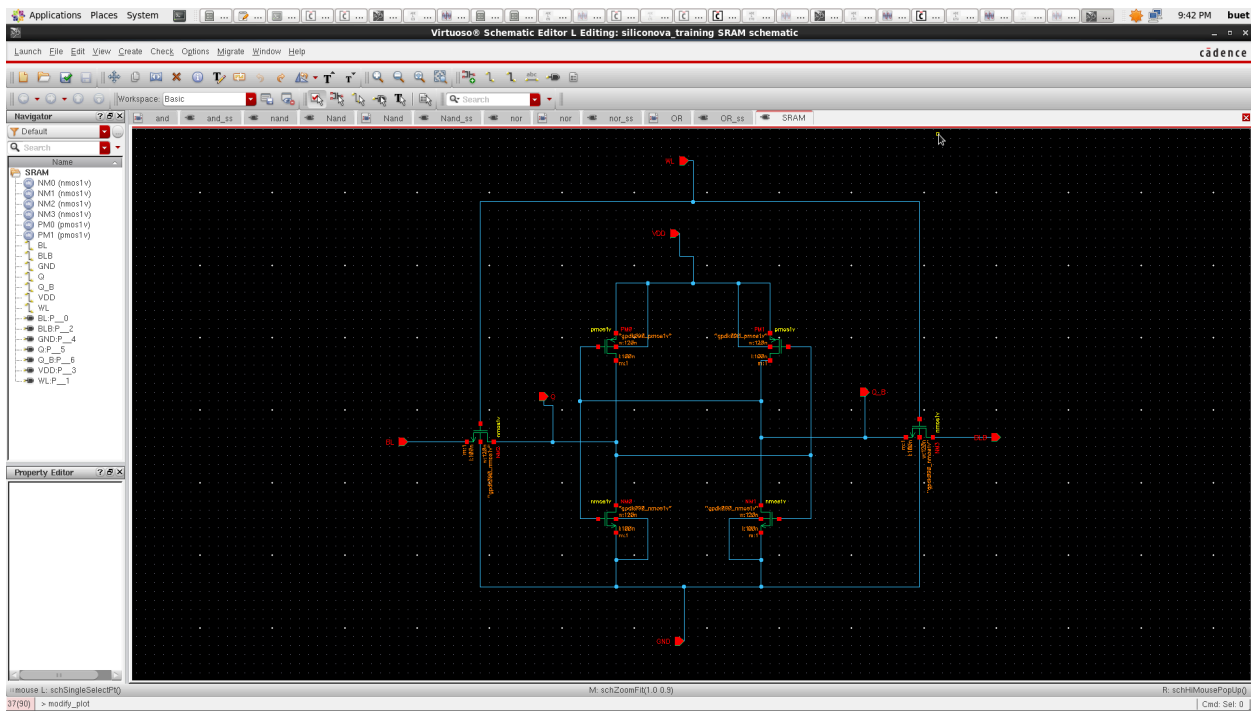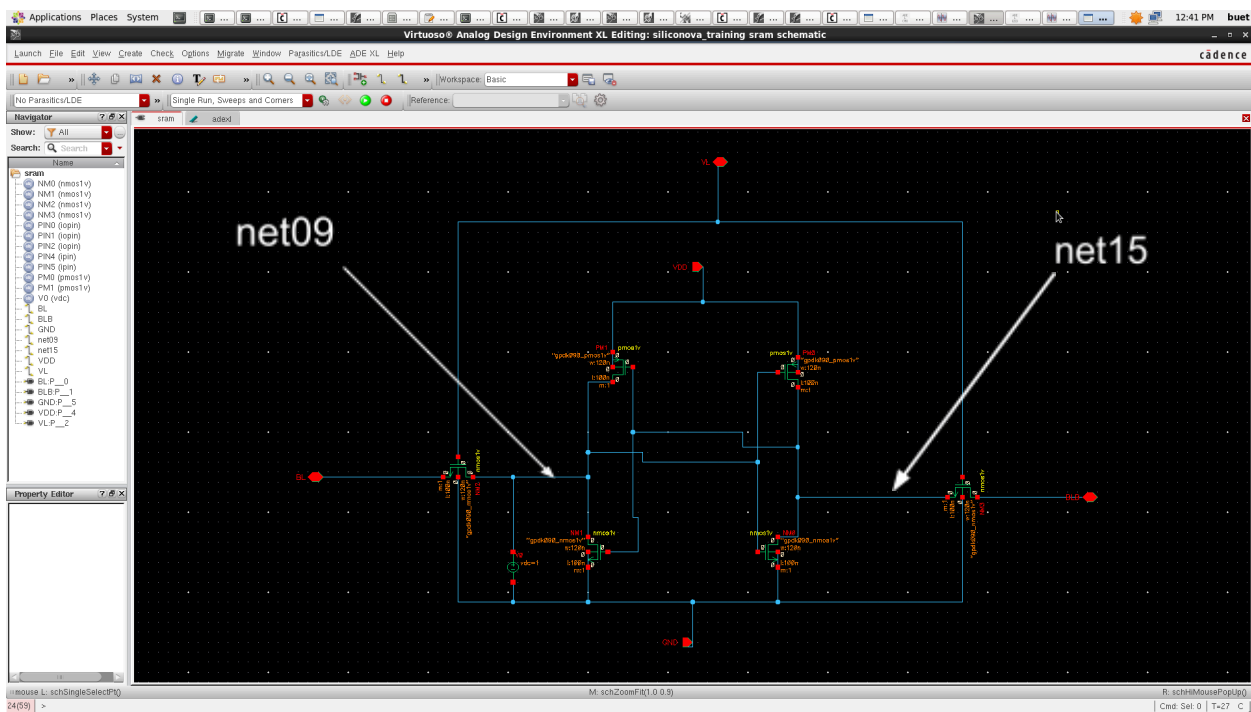


Symbol:

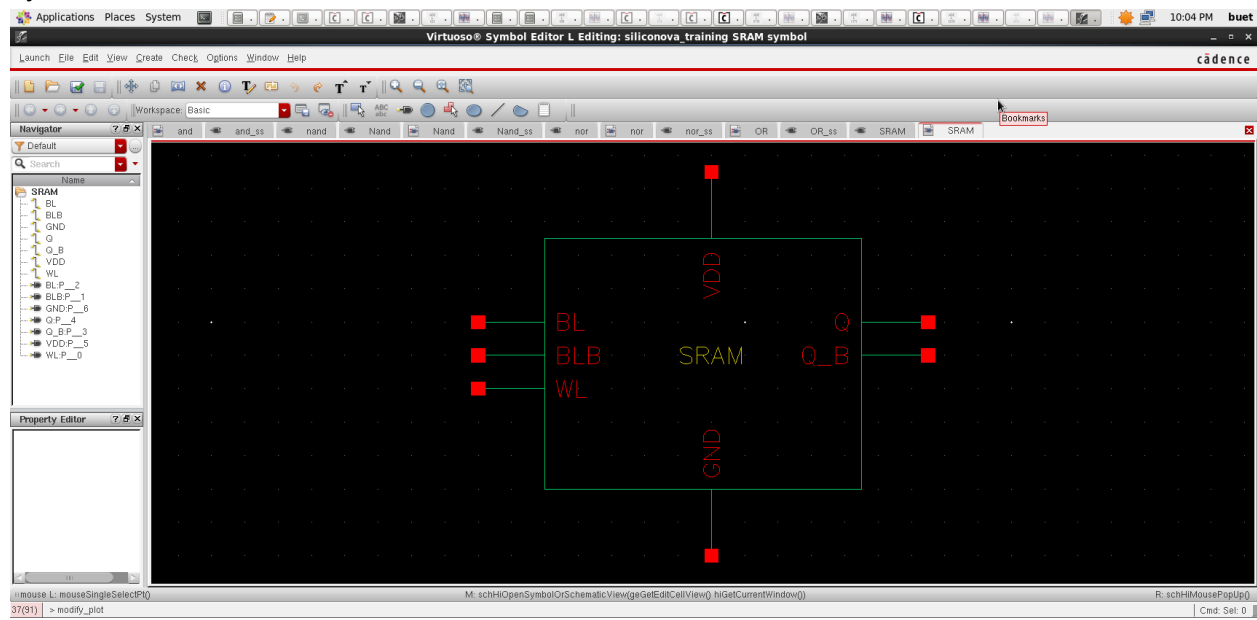


Testbench:

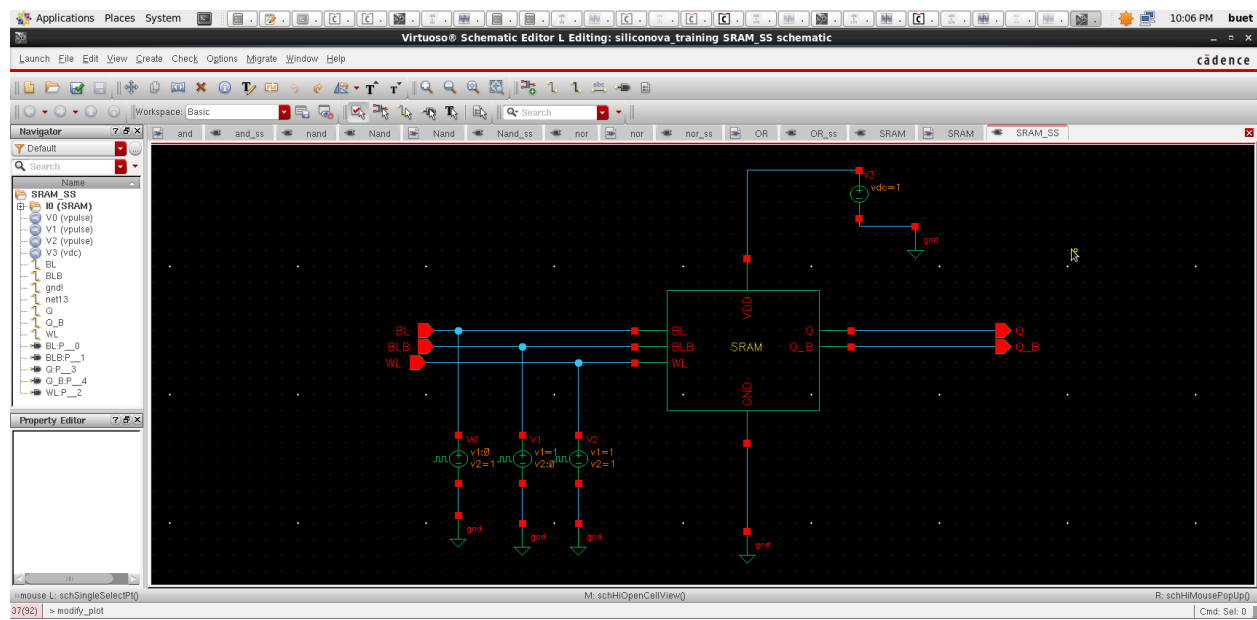


## Output: Output of Transient Analysis

 


## Output: Output for DC analysis

 


## Butterfly Graph:

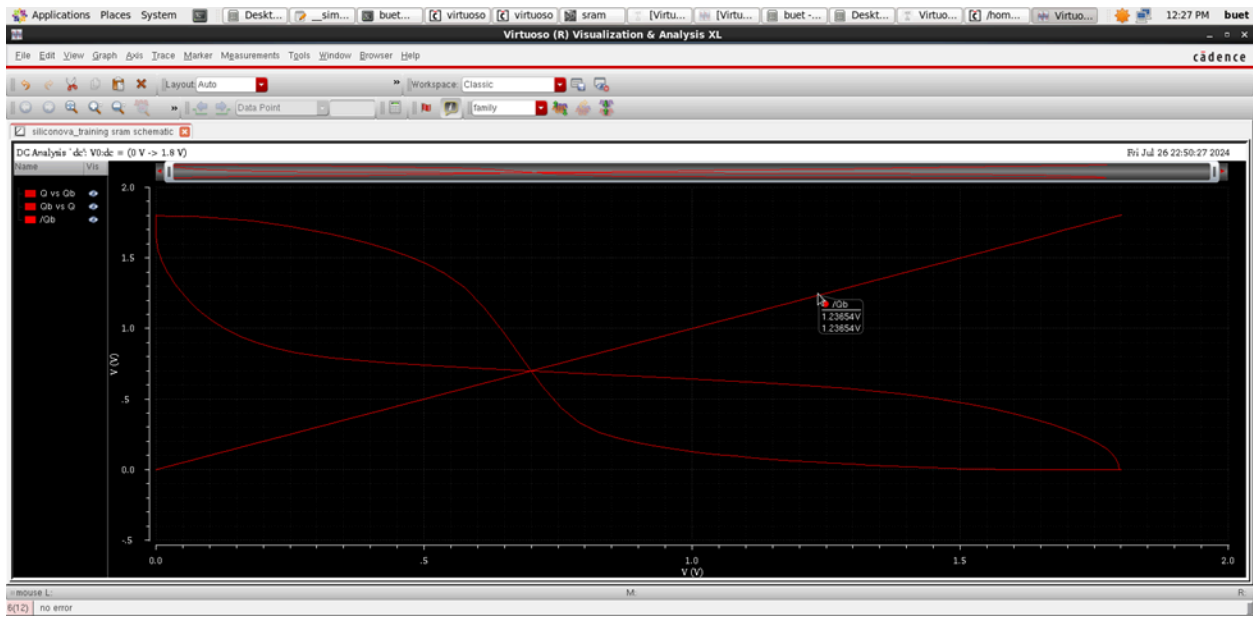

# D Flip Flop

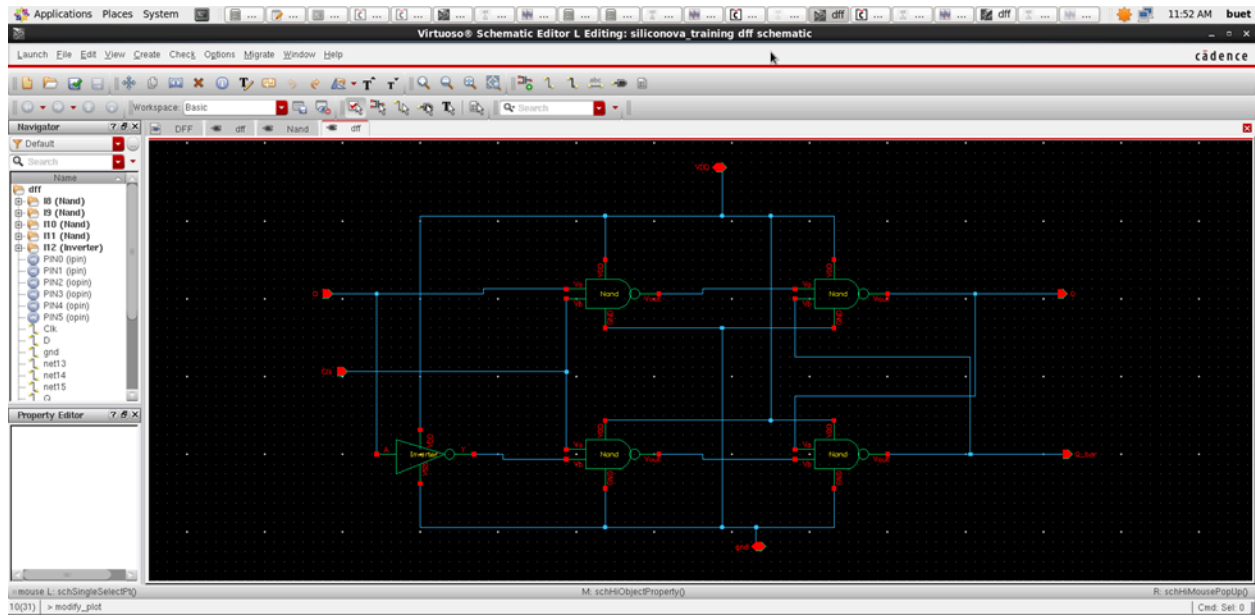


Symbol of D Flip Flop:

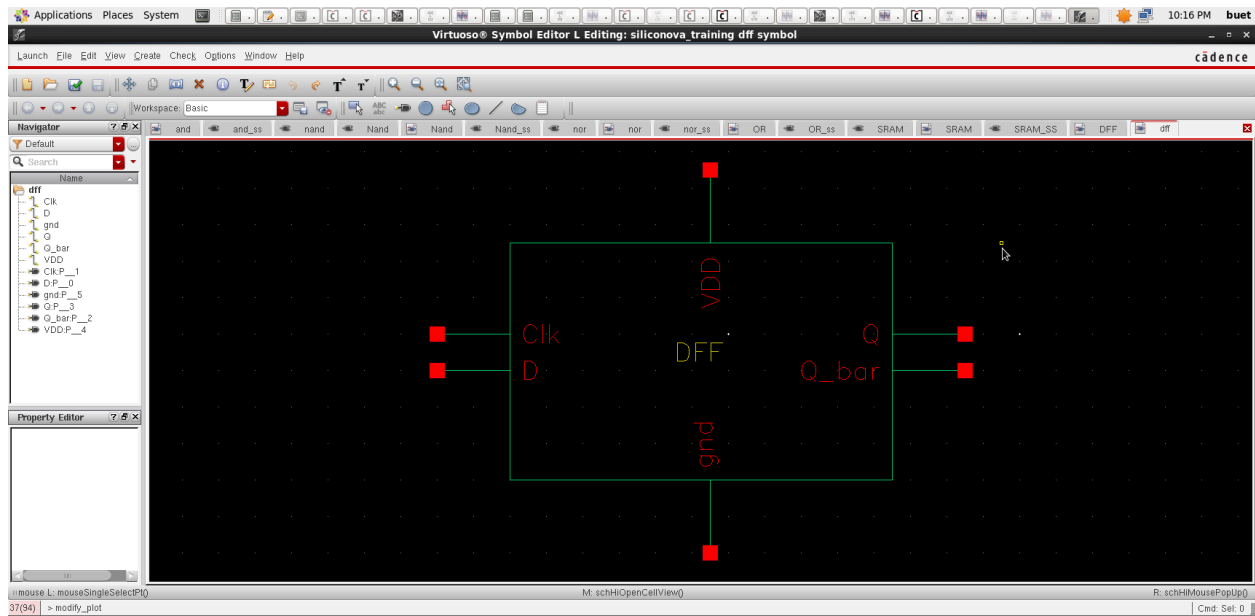



## Testbench

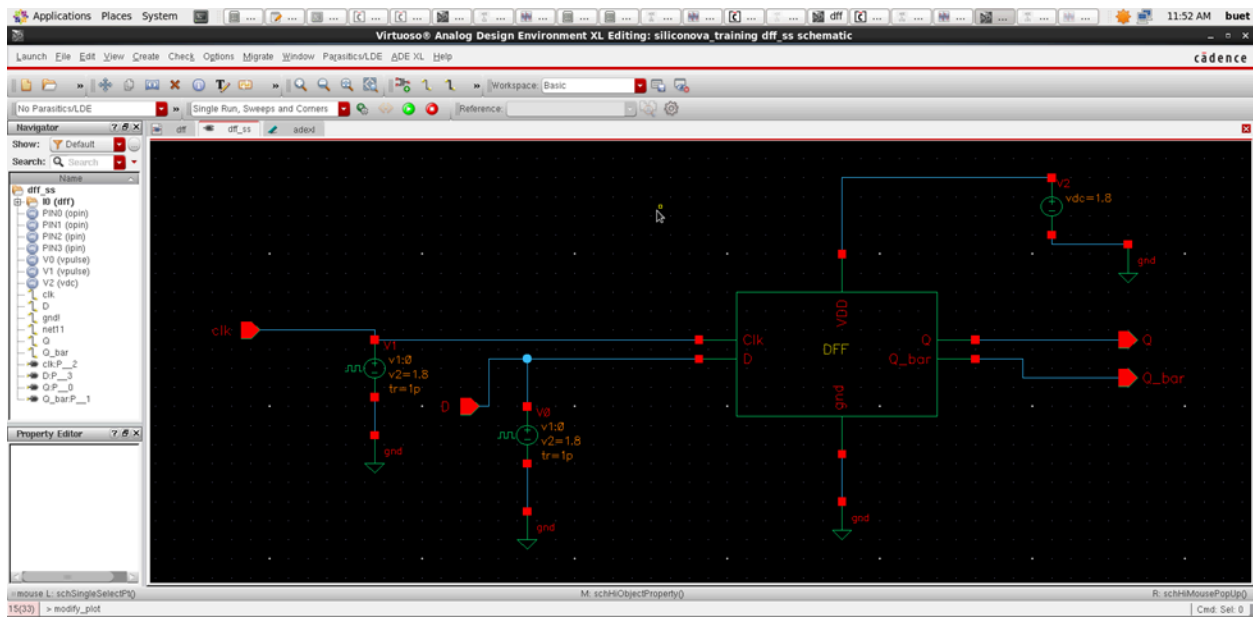

## Output: Transient Analysis

